


ASSIGNMENT 1

AUTOMATIC NIGHT LAMP BEGINNER

Components:

- 1 x Mini Breadboard
- 1 x Arduino UNO R3
- 1 x LDR Photoresistor Sensor
- 2 x 1 k Ω resistors
- 1 x Red LED

Circuit Diagram:

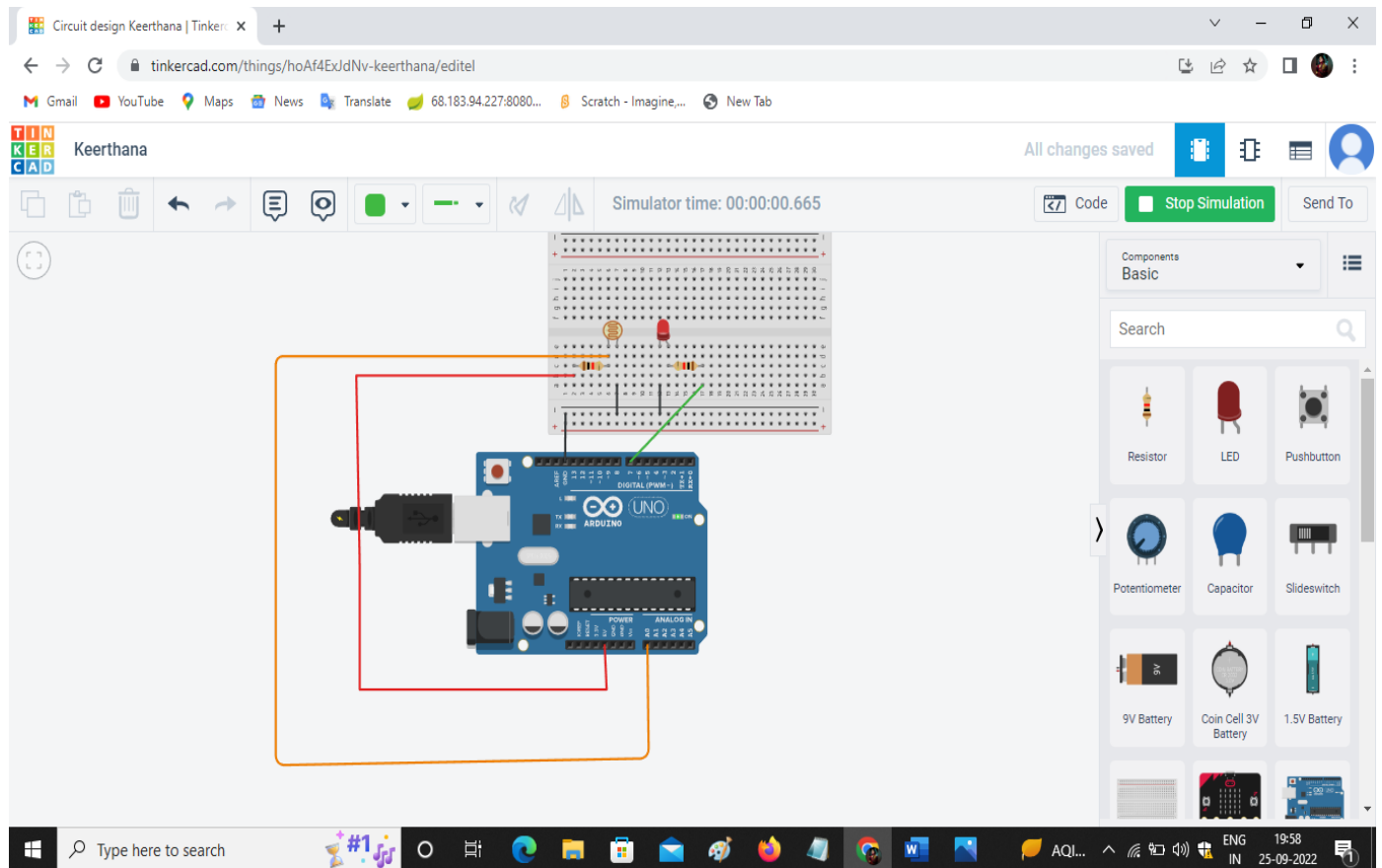

This circuit will be used for automatic night Lamp Turn ON/Turn OFF. When there is no sunlight then lamp (LED) glows and When there is sunlight then lamp (LED) does not glow.

Program:

```
void setup()
{
  Serial.begin(9600);
  pinMode(7,OUTPUT);

void loop()
{
  int c = analogRead(A0) ;
  Serial.println(c) ;
  if(c<500)
  {
    digitalWrite(7,LOW) ;
  }
  else
  {
    digitalWrite(7,HIGH) ;
  }
}
```